
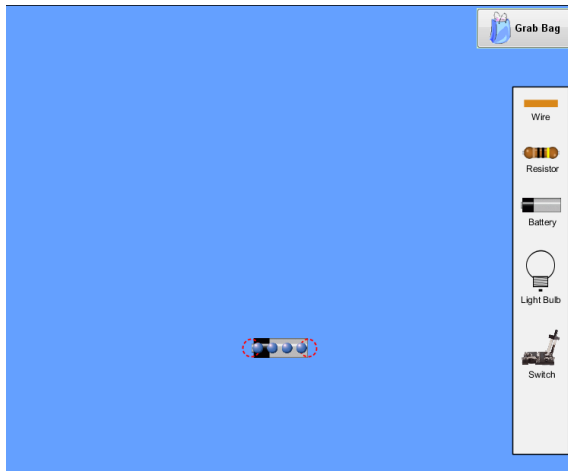


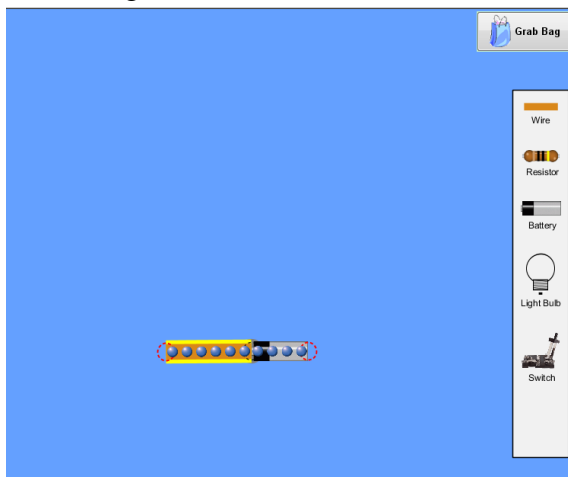The first thing you need to make the circuit work is a battery. Drag a battery into the lower middle of the blue screen.




Right-click on the battery and change the voltage to 100


Next, drag a wire so that it connects to the left side of the battery



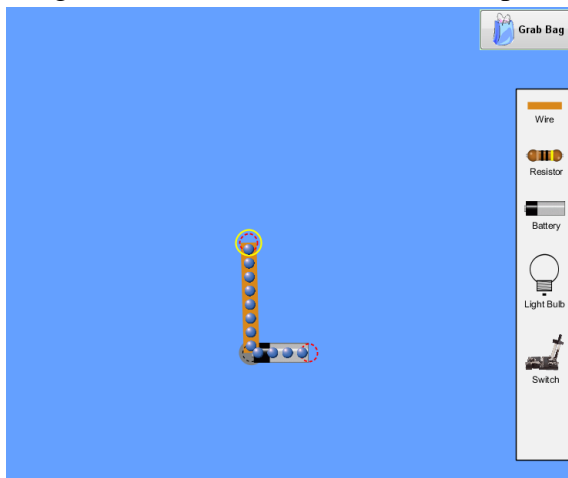
Drag the free end of the wire so that it points up instead of left



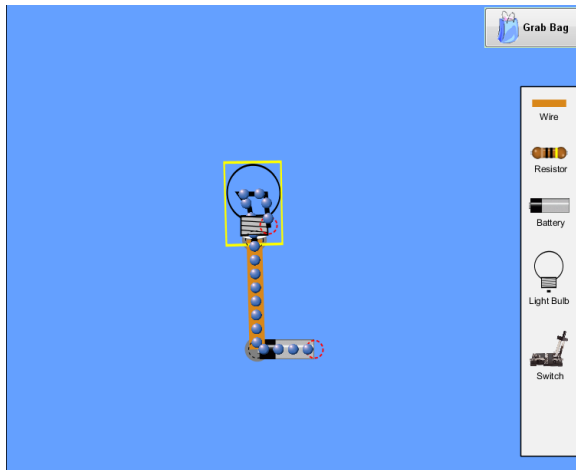
Drag a light bulb to the free end of the wire



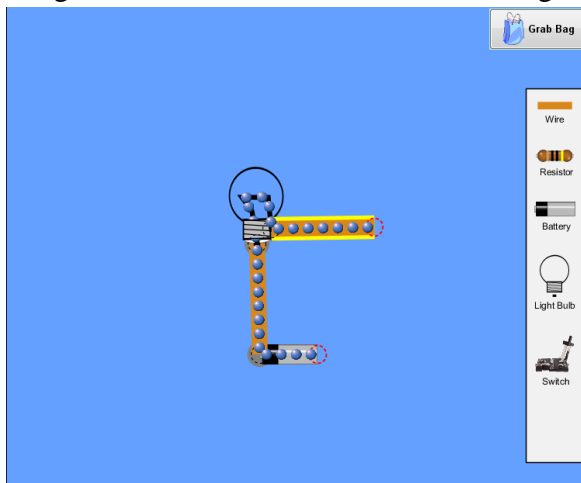
Drag another wire to the free end of the light bulb



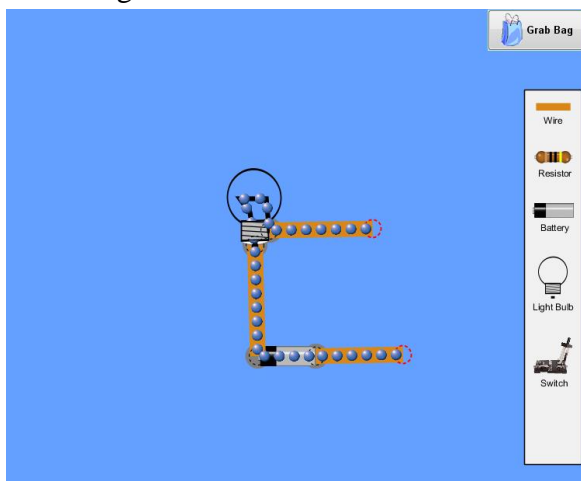
Now drag one more wire to the free end of the battery



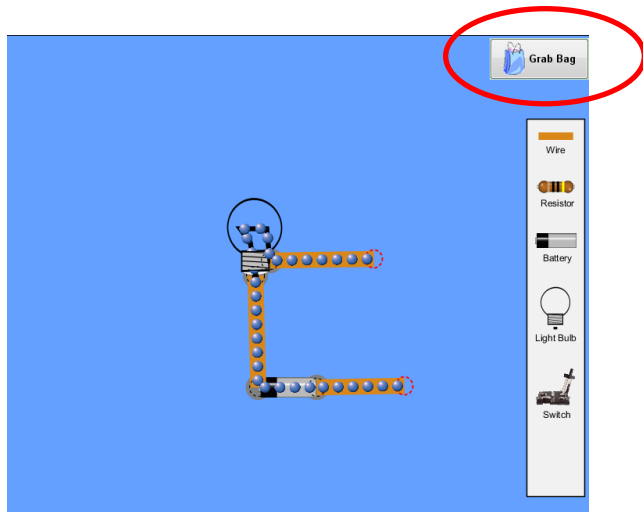Click on the grab bag and select an item to test



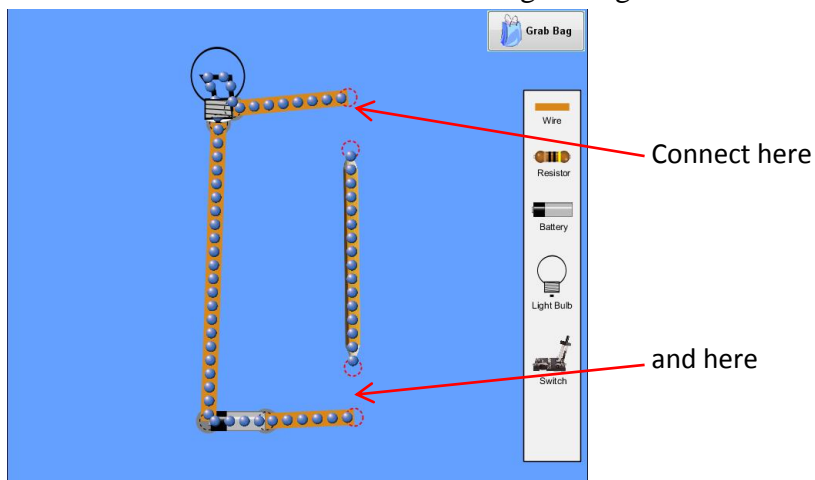Connect either end of the item from the grab bag to the two free wires to complete the circuit



Right click on the item to remove it

Repeat for each item in the grab bag